

# Laboratorio AD\_SAR

---

## Electrónica Digital

**Nievas Aramayo, Pablo Agustín**

**16/06/2020**

Profesor: Agustín Laprovitta

Documento con el desarrollo del laboratorio del conversor analógico a digital usando la herramienta Quartus 2 con código descriptivo VHDL.

# Índice

Índice .....	1
AD_SAR: Elementos .....	2
Modulo: saadc_fsm.....	2
Modulo: shiftreg.....	3
Modulo: approx_reg.....	4
Modulo: SAR.....	5
Modulo: latch.....	6
Modul: AD_SAR .....	7

## AD\_SAR: Elementos

El AD\_SAR está compuesto de dos grandes bloques, el SAR y el latch. Mientras que el latch puede ser descrito fácilmente como un único elemento el SAR está compuesto de varios elementos internos. Estos últimos son: saadc\_fsm, shiftreg, approx\_reg, y una OR. La OR estará implementada en el mismo VHDL que se juntaran todos los elementos del SAR, y los demás tendrán su propio VHDL que serán módulos que el SAR llame.

En los siguientes puntos se mostrara el código VHDL, junto con su RTL y después su test bench.

### Modulo: saadc\_fsm

Código:

```
library ieee;
use ieee.std_logic_1164.all;

entity saadc_fsm is
    port(
        clk      : in  std_logic;
        reset_bar : in  std_logic;
        soc      : in  std_logic;
        last_bit  : in  std_logic;
        load     : out std_logic;
        en       : out std_logic;
        en2      : out std_logic;
        eoc      : out std_logic;
    );
end entity;

architecture rtl of saadc_fsm is



    type state_type is (idle, initial, shift);
    signal state : state_type;

begin

    process (clk, reset_bar, last_bit, soc)
    begin
        if reset_bar = '0' then
            state <= idle;
        elsif (rising_edge(clk)) then
            case state is
                when idle =>
                    if soc = '1' then
                        state <= initial;
                    else
                        state <= idle;
                    end if;
                when initial =>
                    state <= shift;
                when shift =>
                    if last_bit = '1' then
                        state <= idle;
                    else
                        state <= shift;
                    end if;
                end case;
            end if;
        end process;


    process (state)
    begin
        case state is
            when idle =>
                en <= '0';
                en2 <= '0';
                eoc <= '1';
                load <= '0';
            when initial =>
                en <= '0';
                en2 <= '0';
                eoc <= '0';
                load <= '1';
            when shift =>
                en <= '1';
                en2 <= '1';
                eoc <= '0';
                load <= '0';
            end case;
        end process;
    end rtl;
```

RTL:

  

Máquina de estado

Test Bench:

 

## Modulo: shiftreg

Codigo VHDL:

```


library ieee;
use ieee.std_logic_1164.all;

entity shiftreg is
    port(
        clk      : in  std_logic;
        clr_bar   : in  std_logic;
        load      : in  std_logic;
        en        : in  std_logic;
        qout      : out std_logic_vector ( 7 downto 0)
    );
end entity;


architecture move of shiftreg is
    -- type state_type is (set, shift, reset);
    -- signal state : state_type;
begin
    process (clk, clr_bar, load)
        variable ok:std_logic_vector(7 downto 0);
    begin
        if (clr_bar='0') then
            ok:="00000000";--state<=reset;
        elsif (rising_edge(clk)) then
            if (load = '1') then
                ok := "10000000";--state<=set;
            elsif (en='1') then
                for i in 0 to 6 loop
                    ok(i):=ok(i+1);
                end loop;--state<=shift;
                ok(7) := '0';
            end if;
            qout<=ok;
        end process;
    end architecture;

```

RTL:

 

Test Bench:

 

## Modulo: approx\_reg

```


library ieee;
use ieee.std_logic_1164.all;
entity approx_reg is
    port(
        reset_bar, load, en2, en1, clk : in std_logic;
        d: in std_logic_vector(7 downto 0);
        qar : out std_logic_vector(7 downto 0)
    );
end entity;

architecture registro of approx_reg is


    -- type state_type is (set, shift, reset);
    -- signal state : state_type;

begin
    process (clk, reset_bar, load)
        variable ok: std_logic_vector(7 downto 0);
    begin
        if (reset_bar='0') then
            ok:="00000000";--state<=reset;
        elsif (rising_edge(clk)) then
            if (load = '1') then
                ok := "00000000";--state<=set;
            elsif (en1='1' AND en2='1') then
                ok:=d;
            end if;
        end if;
        qar<=ok;
    end process;

end architecture;
    
```

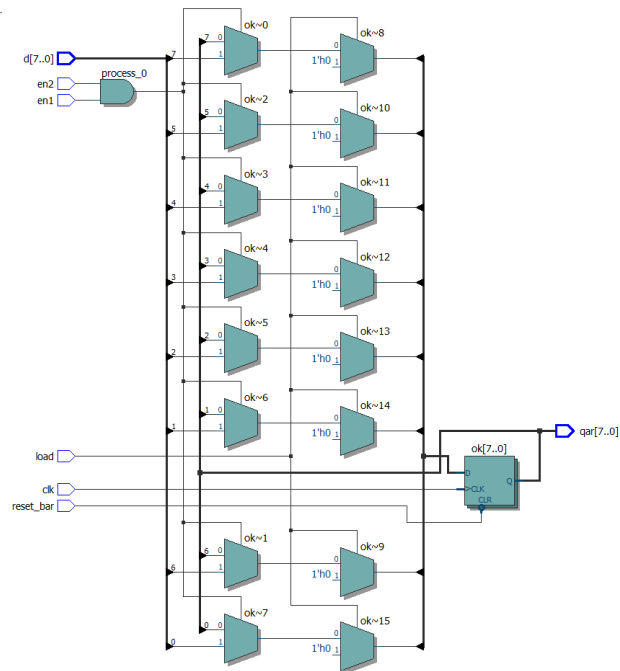

### Test Bench:

 

## Modulo: SAR

Código VHDL:

```

library ieee;
use ieee.std_logic_1164.all;

entity SAR is

    port(
        reset_bar,soc,comp_in,clk : in std_logic;
        eccout std_logic;
        result : out std_logic_vector(7 downto 0)
    );
end entity;

architecture modulation of SAR is
    signal load_signal : std_logic;
    signal en_signal : std_logic;
    signal end_signal : std_logic;
    signal qout_signal : std_logic_vector(7 downto 0);
    signal qar_signal : std_logic_vector(7 downto 0);
    signal or_out : std_logic_vector(7 downto 0);

begin
    estados: entity work.saadd_fem port map( clk => clk,
        reset_bar => reset_bar,
        soc => soc,
        last_bit => qout_signal(0),
        load => load_signal,
        en => en_signal,
        end => end_signal,
        ecc => ecc
    );

    shiftee: entity work.shiftrreg port map( clk => clk,
        clk_bar => reset_bar,
        load => load_signal,
        en => en_signal,
        qout => qout_signal
    );

    registro: entity work.approx_reg port map( clk => clk,
        reset_bar => reset_bar,
        load => load_signal,
        en1 => comp_in,
        end2 => end_signal,
        qar => qar_signal,
        d => or_out
    );


    or_out <= qout_signal OR qar_signal;

    result <= or_out;


end modulation;

```

RTL:

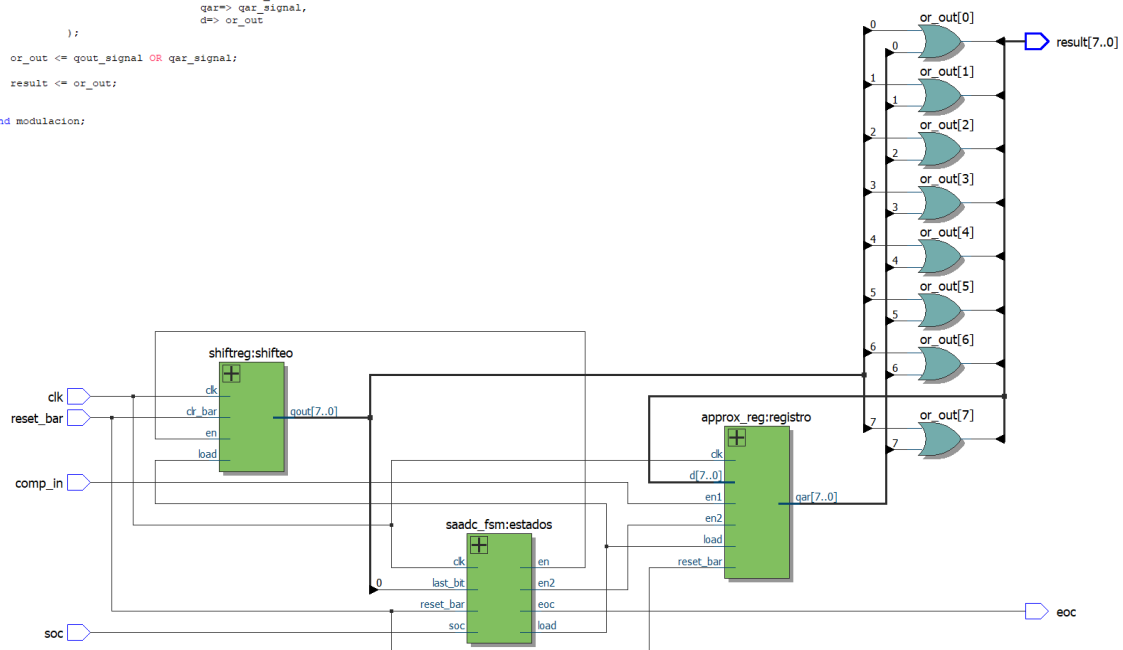

Test Bench:

 


## Modulo: latch


Codigo VHDL:

```
library ieee;
use ieee.std_logic_1164.all;
entity xlatch is
    port(
        reset_bar,le: in std_logic;
        d_in : in std_logic_vector(7 downto 0);
        q: out std_logic_vector(7 downto 0)
    );
end entity;
architecture save of xlatch is
begin
    process(reset_bar,le)
    begin
        if (reset_bar='0') THEN
            q <= "00000000";
        elsif (le = '1') then
            q <= d_in;
        end if;
    end process;
end save;
```

RTL:

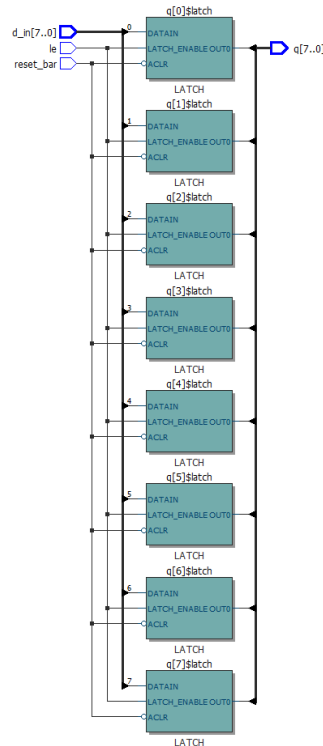

Test Bench:

 

## Modul: AD\_SAR

Código VHDL:

```
library ieee;
use ieee.std_logic_1164.all;

entity AD_SAR is
    port(
        reset_bar,soc,comp_in,clk : in std_logic;
        eoc:out std_logic;
        AD_result,digital_in : out std_logic_vector(7 downto 0)
    );
end entity;

architecture todo of AD_SAR is

    signal eoc_signal          : std_logic;
    signal result_signal       : std_logic_vector (7 downto 0);

begin
    casitodo:  entity work.SAR port map( clk => clk,
        reset_bar => reset_bar,
        soc => soc,
        eoc => eoc_signal,
        comp_in => comp_in,
        result=> result_signal
    );


    guarda: entity work.xlatch port map( reset_bar => reset_bar,
        d_in => result_signal,
        le => eoc_signal,
        q => AD_result
    );

    eoc<=eoc_signal;

    digital_in<=result_signal;

end todo;
```

RTL:

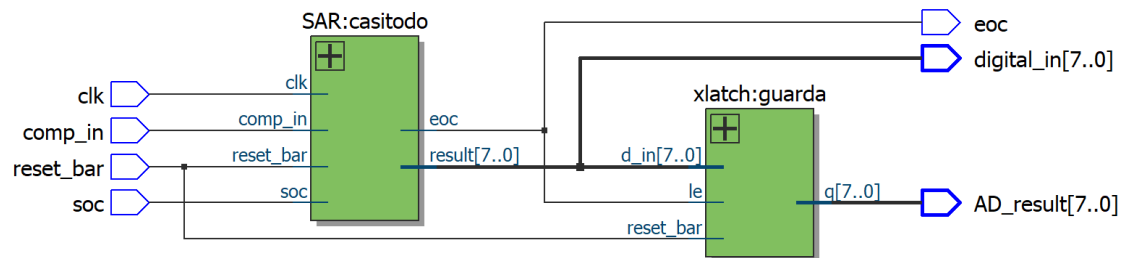

Test Bench:

